
Trabajo Practica Virtual 1.2


Nombre: Luis Morales

Fecha: 29/11/2023


DISEÑO DEL CIRCUITO

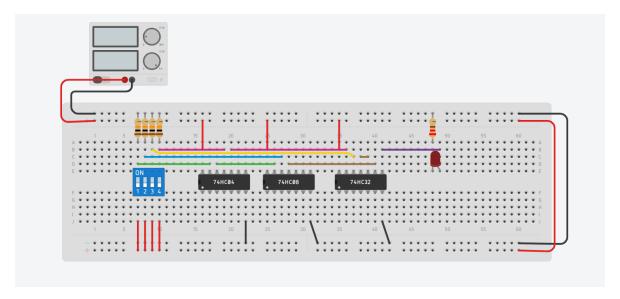

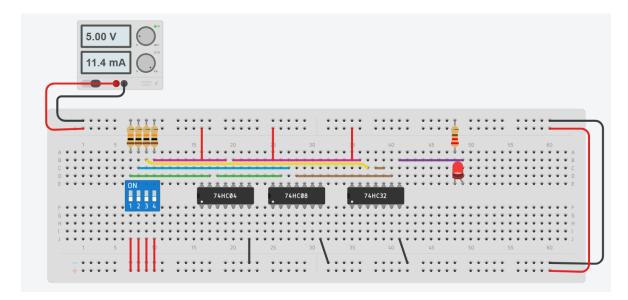
1) Caso: cuando (A = 0) (B = 0) (C = 0) (D = 0) el valor de x = 1



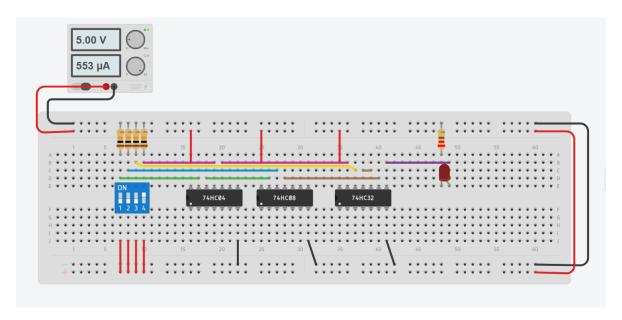
2) Caso: cuando (A = 0) (B = 0) (C = 0) (D = 1) el valor de x = 0



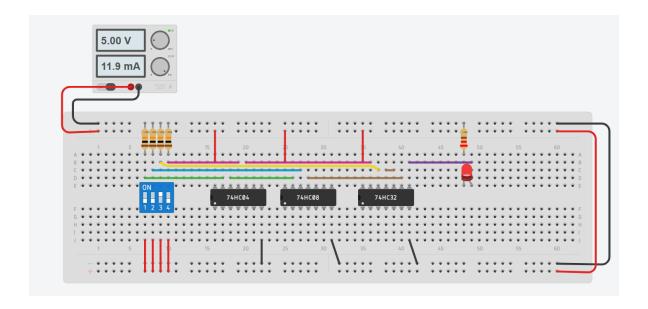
3) Caso: cuando (A = 0) (B = 0) (C = 1) (D = 0) el valor de x = 1



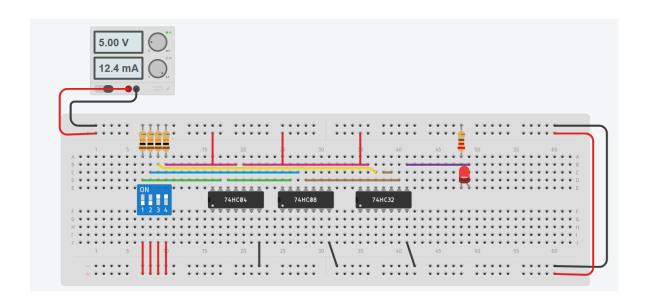
4) Caso: cuando (A = 0) (B = 0) (C = 1) (D = 1) el valor de x = 1



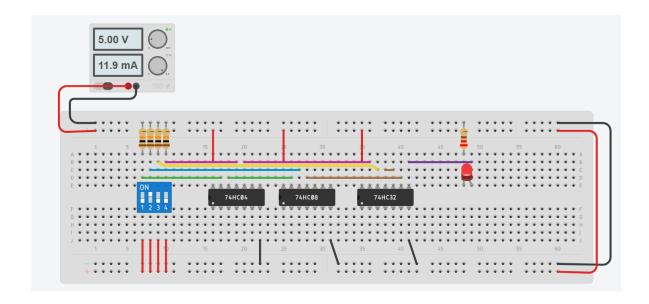
5) Caso: cuando (A = 0) (B = 1) (C = 0) (D = 0) el valor de x = 1



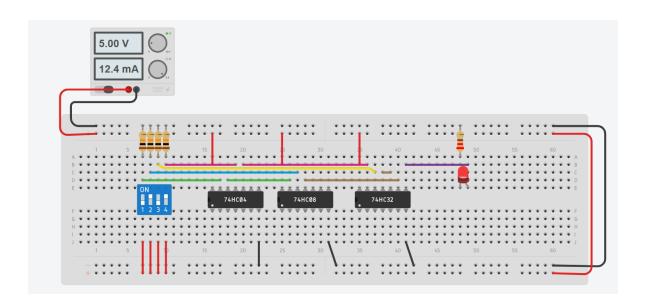
6) Caso: cuando (A = 0) (B = 1) (C = 0) (D = 1) el valor de x = 1



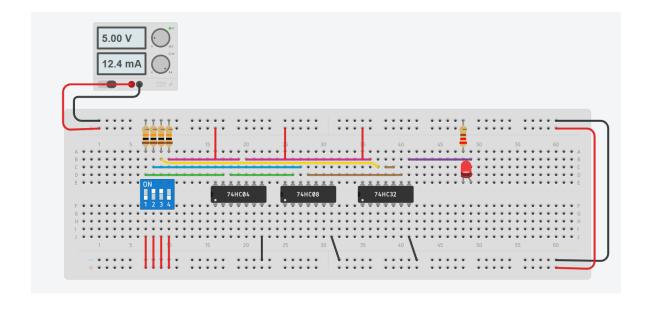
7) Caso: cuando (A = 0) (B = 1) (C = 1) (D = 0) el valor de x = 1



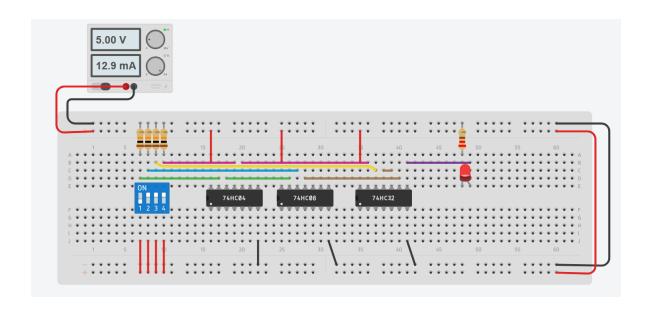
8) Caso: cuando (A = 0) (B = 1) (C = 1) (D = 1) el valor de x = 1



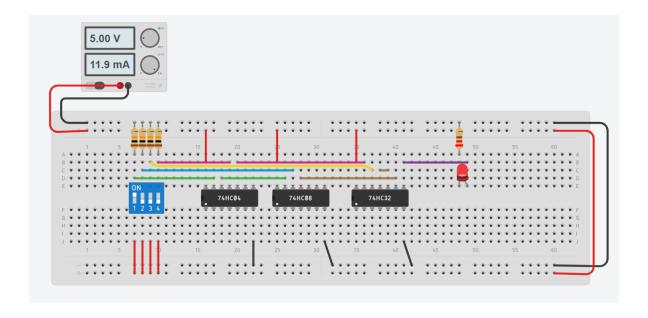
9) Caso: cuando (A = 1) (B = 0) (C = 0) (D = 0) el valor de x = 1



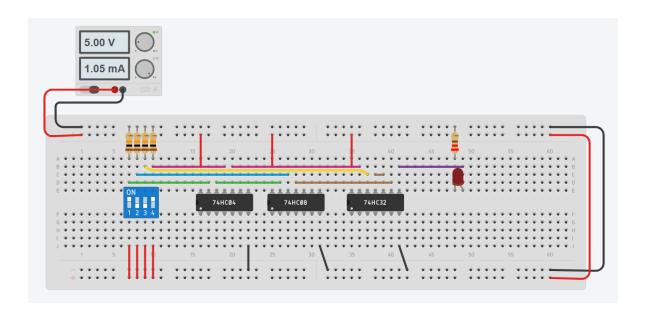
10) Caso: cuando (A = 1) (B = 0) (C = 0) (D = 1) el valor de x = 0



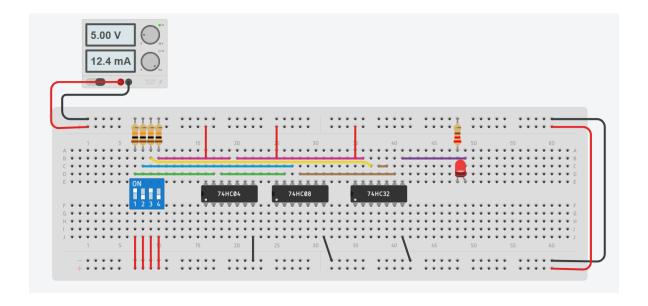
11) Caso: cuando (A = 1) (B = 0) (C = 1) (D = 0) el valor de x = 1



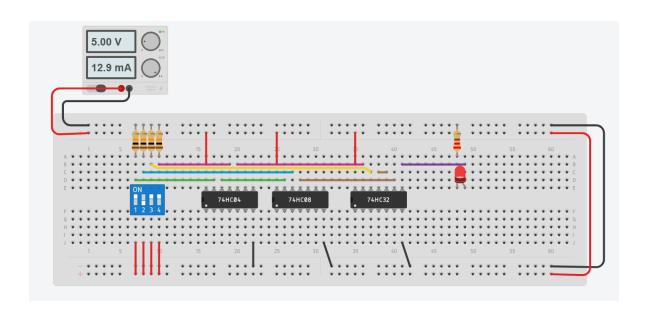
12) Caso: cuando (A = 1) (B = 0) (C = 1) (D = 1) el valor de x = 1



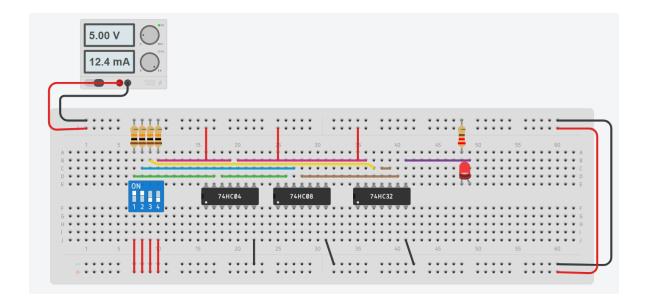
13) Caso: cuando (A = 1) (B = 1) (C = 0) (D = 0) el valor de x = 1



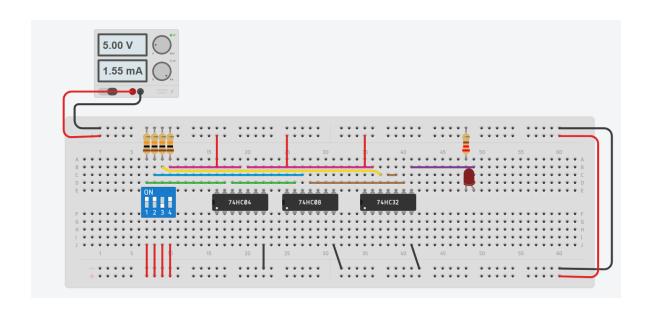14) Caso: cuando (A = 1) (B = 1) (C = 0) (D = 1) el valor de x = 0



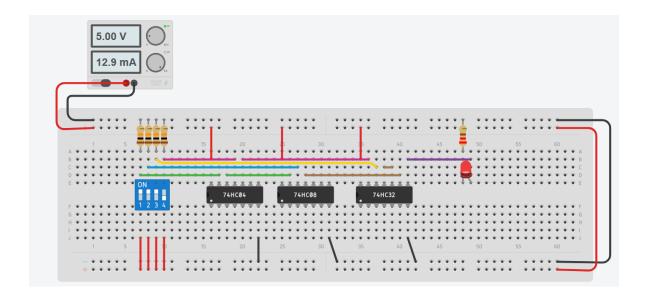15) Caso: cuando (A = 1) (B = 1) (C = 1) (D = 0) el valor de x = 1



16) Caso: cuando (A = 1) (B = 1) (C = 1) (D = 1) el valor de x = 1

